

Introduction to Digital Systems

Part III (Sequential Components)

2022/2023

Analysis of Clocked Synchronous
Finite State Machines

Arnaldo Oliveira, Augusto Silva, Ioulia Skliarova

Lecture Contents

- Analysis of Clocked Synchronous Finite State Machines
 - Typical structure
 - Mealy machine
 - Moore machine
 - Next state and output logic
 - State, transition and output tables
 - State diagrams
 - Timing analysis


Figures and most content extracted from: John F. Wakerly,
“Digital Design – Principles and Practices”, 4 ed., Pearson –
Prentice Hall, 2006 (chapter 7). Reading chapter 7 (4th ed.) or
chapter 10 (5th ed.) is highly recommended.

Clocked Synchronous Finite State Machines

- Why?
 - “Finite State Machine” (FSM)
 - “Clocked”
 - “Synchronous”
- State change at clock “tick”

FSM Structure (Mealy Machine)

Figure 7-35 Clocked synchronous state-machine structure (Mealy machine).

 


$$\text{next state} = F(\text{current state}, \text{inputs})$$

$$\text{outputs} = G(\text{current state}, \text{inputs})$$

FSM Structure (Moore Machine)

Figure 7-36 Clocked synchronous state-machine structure (Moore machine).

 

$$\text{next state} = F(\text{current state}, \text{inputs})$$

$$\text{outputs} = G(\text{current state})$$

Latches and Flip-flops

Characteristic Equations

- Characteristic Equation – what is the next state depending on current state and input(s)?

<i>Device Type</i>	<i>Characteristic Equation</i>
S-R latch	$Q^* = S + R' \cdot Q$
D latch	$Q^* = D$
Edge-triggered D flip-flop	$Q^* = D$
D flip-flop with enable	$Q^* = EN \cdot D + EN' \cdot Q$

Table 7-1
Latch and flip-flop
characteristic
equations.

Clocked Synchronous FSM Analysis


The analysis of a clocked synchronous state machine has three basic steps:

1. Determine the next-state and output functions F and G .
2. Use F and G to construct a *state/output table* that completely specifies the next state and output of the circuit for every possible combination of current state and input.
3. (Optional) Draw a *state diagram* that presents the information from the previous step in graphical form.


state/output table

state diagram

Figure 7-35 Clocked synchronous state-machine structure (Mealy machine).

 

Example of an FSM Logic Circuit

 

Mealy
or
Moore?

Figure 7-38 Clocked synchronous state machine using positive-edge-triggered D flip-flops.

Example of an FSM Logic Circuit

Excitation equations

$$D_0 = Q_0 \cdot EN' + Q_0' \cdot EN$$

$$D_1 = Q_1 \cdot EN' + Q_1' \cdot Q_0 \cdot EN + Q_1 \cdot Q_0' \cdot EN$$

Characteristic equations


$$Q_0^* = D_0$$

$$Q_1^* = D_1$$

Transition equations

$$Q_0^* = Q_0 \cdot EN' + Q_0' \cdot EN$$
 
$$Q_1^* = Q_1 \cdot EN' + Q_1' \cdot Q_0 \cdot EN + Q_1 \cdot Q_0' \cdot EN$$



Output(s)
equation(s)

$$MAX = Q_1 \cdot Q_0 \cdot EN$$

Figure 7-38 Clocked synchronous state machine using positive-edge-triggered D flip-flops.

Transition, State and State/Output Tables

Transition equations

$$Q_0^* = Q_0 \cdot EN' + Q_0' \cdot EN$$

$$Q_1^* = Q_1 \cdot EN' + Q_1' \cdot Q_0 \cdot EN + Q_1 \cdot Q_0' \cdot EN$$

Output(s)
equation(s)

$$MAX = Q_1 \cdot Q_0 \cdot EN$$

What is the purpose of the circuit and the role of its inputs and outputs?

		EN	
<i>Q₁</i>	<i>Q₀</i>	0	1
00	00	01	
01	01	10	
10	10	11	
11	11	00	
		Q _{1*} Q _{0*}	

		EN	
		S	0
<i>S</i>		0	1
A	A	B	
B	B	C	
C	C	D	
D	D	A	
		S*	

		EN	
<i>S</i>		0	1
A	A, 0	B, 0	
B	B, 0	C, 0	
C	C, 0	D, 0	
D	D, 0	A, 1	
		S*, MAX	


Table 7-2

Transition, state, and state/output tables for the state machine in Figure 7-38.


State Diagram for a Mealy Machine

s	EN	
	0	1
A	A, 0	B, 0
B	B, 0	C, 0
C	C, 0	D, 0
D	D, 0	A, 1
S*, MAX		

Figure 7-39
State diagram
corresponding to the
state machine of
Table 7-2.

 

Outputs in a Moore Machine

 

$$\text{MAXS} = Q_0 \cdot Q_1$$


Outputs in a Moore Machine

Table 7-3
State/output table for
a Moore machine.

S	EN		MAXS
	0	1	
A	A	B	0
B	B	C	0
C	C	D	0
D	D	A	1

S*

State Diagram for a Moore Machine

 

EN		MAXS
S	0	1
A	A	B
B	B	C
C	C	D
D	D	A
		1
	S*	

Figure 7-40
State diagram
corresponding to the
state machine of
Table 7-3.

Redrawn Logic Diagram

Transition equations


$$Q0^* = Q0 \cdot EN' + Q0' \cdot EN$$

$$Q1^* = Q1 \cdot EN' + Q1' \cdot Q0 \cdot EN + Q1 \cdot Q0' \cdot EN$$

Output(s)
equation(s)

$$MAX = Q1 \cdot Q0 \cdot EN$$

Figure 7-41 Redrawn logic diagram for a clocked synchronous state machine.

 

Timing Diagram



 


Figure 7-42 Timing diagram for example state machine.

 

Cascading Two Counters

Using MAX output

 

Using MAXS output


 


Figure 7-42 Timing diagram for example state machine.


 


Timing Analysis

- Purpose
 - Obtain all the circuit delays with the aim of determine the maximum operating frequency
- Ideal vs. real circuits
 - Real circuits exhibit propagation, setup and hold times
 - In ideal circuits all these timing parameters are zero
- Simplifications
 - Single clock domain fully synchronous circuits
 - Flip-flop “hold time” lower than both propagation times (T_{pLH} and T_{pHL})

Timing Analysis - A Simple Example

  - Flip-flop(s) without combinatorial logic in between / in the feedback path
- What is the maximum operating frequency / minimum period of CLK?





T_{min} when $T_{slack} = 0$

$$T_{min} = \max(T_{pHL}, T_{pLH}) + T_{setup}$$

$$f_{max} = \frac{1}{T_{min}}$$



Timing Analysis - Another Example

  - Flip-flop(s) with simple logic gate in between / in the feedback path
- What is the maximum operating frequency / minimum period of CLK?



$$T_{min} \text{ when } T_{slack} = 0 \quad T_{min} = \max(T_{pHL}, T_{pLH}) + T_{gate} + T_{setup} \quad f_{max} = \frac{1}{T_{min}}$$

Synchronous Circuit General Structure

  

What is the maximum operating frequency / minimum period of CLK?

$$T_{min} \text{ when } T_{slack} = 0$$

$$T_{min} = \max(T_{pHL}, T_{pLH}) + T_{criticalpath} + T_{setup}$$

$$f_{max} = \frac{1}{T_{min}}$$

FSM Timing Analysis

 


Figure 7-38 Clocked synchronous state machine using positive-edge-triggered D flip-flops.

$$T_{\min} = ?$$
$$f_{\max} = ?$$

Consider:

$$T_{pHL} = 4 \text{ ns}$$

$$T_{pLH} = 5 \text{ ns}$$

$$T_{\text{setup}} = 3 \text{ ns}$$

$$T_{\text{hold}} = 1 \text{ ns}$$

$$T_{\text{gate}} = 4 \text{ ns}$$

(assume that all gates exhibit the same delay)

Another FSM Example

 


Figure 7-43 A clocked synchronous state machine with three flip-flops and eight states.

Another FSM Example

Excitation Equations

$$D_0 = Q_1' \cdot X + Q_0 \cdot X' + Q_2$$

$$D_1 = Q_2' \cdot Q_0 \cdot X + Q_1 \cdot X' + Q_2 \cdot Q_1$$

$$D_2 = Q_2 \cdot Q_0' + Q_0' \cdot X' \cdot Y$$

 


Figure 7-43 A clocked synchronous state machine with three flip-flops and eight states.

Another FSM Example

Transition Equations

$$Q0^* = Q1' \cdot X + Q0 \cdot X' + Q2$$

$$Q1^* = Q2' \cdot Q0 \cdot X + Q1 \cdot X' + Q2 \cdot Q1$$

$$Q2^* = Q2 \cdot Q0' + Q0' \cdot X' \cdot Y$$

 


Figure 7-43 A clocked synchronous state machine with three flip-flops and eight states.

Another FSM Example

Output Equations

 


Figure 7-43 A clocked synchronous state machine with three flip-flops and eight states.

Another FSM Example – Transition / Output and State / Output Tables

$$Q_0^* = Q_1' \cdot X + Q_0 \cdot X' + Q_2$$

$$Q_1^* = Q_2' \cdot Q_0 \cdot X + Q_1 \cdot X' + Q_2 \cdot Q_1$$

$$Q_2^* = Q_2 \cdot Q_0' + Q_0' \cdot X' \cdot Y$$

$$Z_1 = Q_2 + Q_1' + Q_0'$$

$$Z_2 = Q_2 \cdot Q_1 + Q_2 \cdot Q_0'$$


Table 7-4
Transition/output
and state/output
tables for the
state machine
in Figure 7-43.

			XY							
			Q2	Q1	Q0	00	01	10	11	Z1 Z2
			000	000	100	001	001	10		
			001	001	001	011	011	10		
			010	010	110	000	000	10		
			011	011	011	010	010	00		
			100	101	101	101	101	11		
			101	001	001	001	001	10		
			110	111	111	111	111	11		
			111	011	011	011	011	11		
			Q2* Q1* Q0*				S*			

Another FSM Example

State Diagram

Figure 7-44 State diagram corresponding to Table 7-4.

 

Conclusion

- At the end of this lecture and corresponding lab, it is fundamental to know how to analyse sequential circuits described by finite state machines and implemented with D type flip-flops, including functional/behavioral and timing aspects
- Plan for the next lectures
 - Synthesis of sequential circuits (Finite State Machines)
 - Standard sequential circuits
 - Registers and shift registers
 - Counters
 - Iterative vs. sequential circuits

Reading chapter 7 (4th ed.) or chapter 10 (5th ed.) of John F. Wakerly, "Digital Design – Principles and Practices", Pearson – Prentice Hall, is highly recommended.